

## Terminology

- Digital: also known as discrete, is a signal that at any time can have one of a finite set of possible values.
- Analog: also known as continuous, is a signal that can have one of an infinite number of possible values.
- Moore's Law: the doubling of IC density every 18 months.
- Sum of Products: an equation written as an ORing of product terms such that no parentheses are present.
- Sum of Minterms: an equation in the sum-of-products form, and every product term is a minterm.
- Equivalent: two functions that return exactly the same results.
- Complement: also known as inverse, such that the outputs of two functions return exactly the opposite results.
- Optimization: a transformation that improves all criteria of interest or improves some of those criteria without worsening the others.
- Tradeoff: a transformation that improves some criteria at the expense of other criteria of interest.
- Critical Path: the longest path from any input to the circuit's output; i.e. sum the amount of processing time for each possible circuit path and whatever path returns the largest value is the critical path.

## Facts

- Digital methods of recording data do not deteriorate over time.
- Digital data can be compressed.
- Custom digital circuits take less processing time than a microprocessor.

## Voltage-to-Binary

t	V	B
0	0	00
1	0	00
2	1	01
3	2	10
4	3	11
5	2	10
6	1	01

V = 0012321

B = 00000110111001

## Binary-to-Decimal

$$(1011)_2 = 1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 1 \times 2^0 = (11)_{10}$$

## Decimal-to-Binary (Addition Method)

$$(65)_{10}$$

$$\begin{array}{r} 1 \quad 0 \quad 0 \quad 0 \quad 0 \quad 1 \\ 64 \quad 32 \quad 16 \quad 8 \quad 4 \quad 2 \quad 1 \end{array}$$

$$64 + 1 = 65 = (1000001)_2$$

## Binary-to-Hexadecimal

(11100111)<sub>2</sub> NOTE: If length of binary string is not equal to a multiple of four, then append zeroes to front of string until it is.

$$(1110)_2 = 1 \times 2^3 + 1 \times 2^2 + 1 \times 2^1 + 0 \times 2^0 = (14)_{10} = (E)_{16}$$

$$(0111)_2 = 0 \times 2^3 + 1 \times 2^2 + 1 \times 2^1 + 1 \times 2^0 = (7)_{10} = (7)_{16}$$

$$(E7)_{16}$$

## Hexadecimal-to-Binary

$$(B0C4)_{16}$$

$$(B)_{16} = (11)_{10} = \frac{1 \quad 0 \quad 1 \quad 1}{8 \quad 4 \quad 2 \quad 1} = (1011)_2$$

$$(0)_{16} = (0)_{10} = \frac{0 \quad 0 \quad 0 \quad 0}{8 \quad 4 \quad 2 \quad 1} = (0000)_2$$

$$(C)_{16} = (12)_{10} = \frac{1 \quad 1 \quad 0 \quad 0}{8 \quad 4 \quad 2 \quad 1} = (1100)_2$$

$$(4)_{16} = (4)_{10} = \frac{0 \quad 1 \quad 0 \quad 0}{8 \quad 4 \quad 2 \quad 1} = (0100)_2$$

$$(1011000011000100)_2$$

## Binary / Decimal / Hexadecimal

B	D	H
0000	00	0
0001	01	1
0010	02	2
0011	03	3
0100	04	4
0101	05	5
0110	06	6
0111	07	7
1000	08	8
1001	09	9
1010	10	A
1011	11	B
1100	12	C
1101	13	D
1110	14	E
1111	15	F

## Prime Numbers

02	03	05	07	11
13	17	19	23	29
31	37	41	43	47
53	59	61	67	71
73	79	83	89	97

## Decimal-to-Base 5

$$(128)_{10} \rightarrow (\dots)_5$$

$$\begin{array}{r} 25 \quad 5 \quad 1 \quad 0 \\ 5 \overline{)128} \quad 5 \overline{)25} \quad 5 \overline{)5} \quad 5 \overline{)1} \\ -125 \quad -25 \quad -5 \quad -0 \\ \hline 3 \quad 0 \quad 0 \quad 1 \end{array}$$

$$(1003)_5$$

## Boolean Algebra Properties

$$a + (b * c) = (a + b) * (a + c)$$

$$a + 0 = a$$

$$a * 1 = a$$

$$a + a' = 1$$

$$a * a' = 0$$

$$a + 1 = 1$$

$$a * 0 = 0$$

$$a + a = a$$

$$a * a = a$$

$$(a + b)' = a'b'$$

$$(ab)' = a' + b'$$

$$F = a + a'b + acd + c' + ab'c'd$$

Variables: a, b, c, d

Literals: a, a', b, a, c, d, c', a, b', c', d

Product Terms: a, a'b, acd, c', ab'c'd

Minterms: ab'c'd

## Multilevel Logic Optimization

### Initial

$$ab + acd + ace$$

$$abcd + abcef$$


### Optimized

$$a(b + c(d + e))$$

$$abc(d + ef)$$

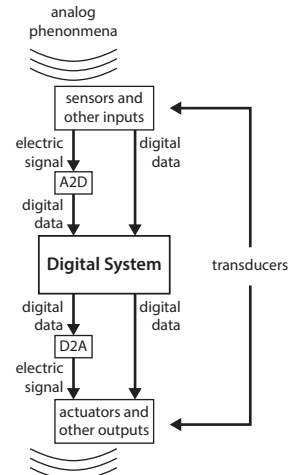
## Circuit Design Metrics

- Performance: a measure of execution time for a computation on the system.
- Size: a measure of the number of transistors, or silicon area, of a digital system.
- Power: a measure of the energy consumed by the system per second, directly relating to both the heat generated by the system and to the battery energy consumed by computations.




$$F = ((a+b')(c'+d)) + (c+d+e')$$

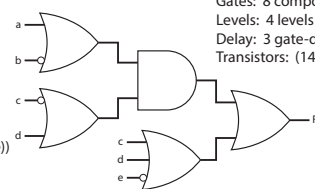
Gates: 8 components  
Levels: 4 levels  
Delay: 3 gate-delays  
Transistors: (14 inputs)\*2 = 28



## K-Map

- Implicants: any legal circle on the K-map.
- Prime Implicants: largest possible legal circles on the K-map.
- Essential Prime Implicants: the largest possible circle that is also the only circle that covers a particular | on the K-map.

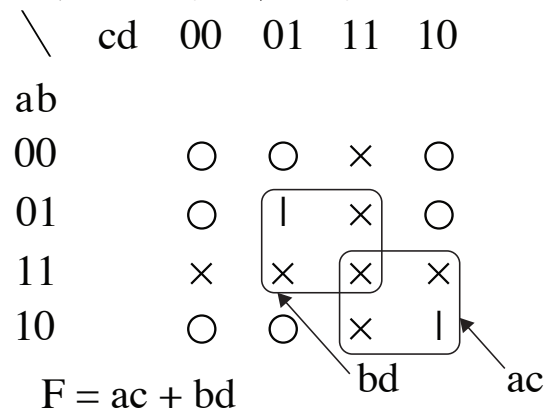

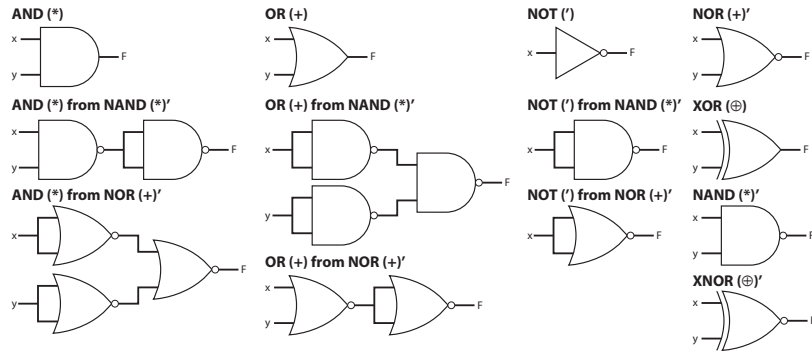

### Boolean Functions

Combinations (Rows):  $2^n$ ,  $n$  = number of variables  
 Functions:  $2^c$ ,  $c$  = number of combinations (rows)

$a$	$b$	$a'$	$b'$	AND $ab$	OR $a+b$	NOR $(a+b)'$	XOR $a \oplus b$	NAND $(ab)'$	XNOR $(a \oplus b)'$
0	0	1	1	0	0	1	0	1	1
0	1	1	0	0	1	0	1	1	0
1	0	0	1	0	1	0	1	1	0
1	1	0	0	1	1	0	0	0	1

### Logic Gate Operations


NOR Detects all 0s  
 XOR Detects odd number of 1s  
 NAND Detects all 1s  
 XNOR Detects even number of 1s

### 4x2 priority encoder


$i3$	$i2$	$i1$	$i0$	$e1$	$e0$
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	0	1	1	0
0	1	1	0	1	1
0	1	1	1	1	1
1	0	0	0	1	1
1	0	0	1	1	1
1	0	1	0	1	1
1	0	1	1	1	1
1	1	0	0	1	1
1	1	0	1	1	1
1	1	1	0	1	1
1	1	1	1	1	1

$$e1 = i3 + i2$$


$$e0 = i3 + i2' i1$$

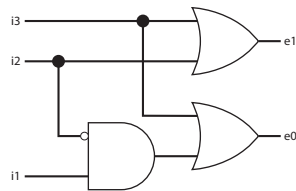

### 2x4 decoder w/ enable

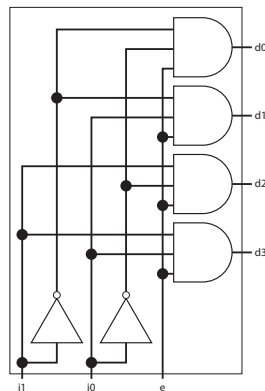

### 4x1 multiplexer

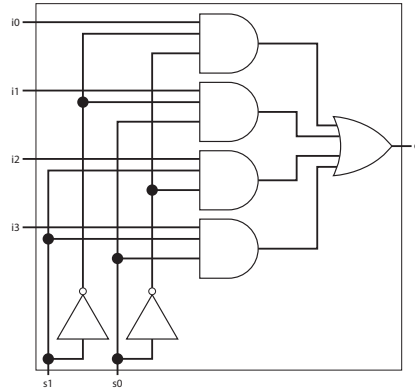

### 4-bit 2x1 mux

