

# Project Proposal

Joel Meine

**Project:** Sequential Multiplier, Shift-and-Add (4-bit)


## Description:

A digital arithmetic component that will execute the multiplication of two 4-bit binary values; thus the component is limited to the product range of 0 - 225 ( $15 * 15 = 225$ ).

## Application:


The function of multiplication is a fundamental and essential operation of mathematics that is widely used within an infinite number of practical, real-world applications. Compared to the array-style multiplier, we see that a trade-off is evident. While the array-style multiplier is much faster than the sequential multiplier, it is also much larger in architecture than the sequential multiplier. Thus we see that if processing speed is a greater priority than physical size of the digital device, the device would incorporate an array-style multiplier(s) resulting in a device that might be considerably large but comparatively fast at computational operations (e.g. a dedicated server). If physical size is a greater priority than the processing speed of the digital device, the device would incorporate a sequential multiplier(s) resulting in a device that might be considerably small but comparatively slow at computational operations (e.g. a smartphone).

## HL Diagram:

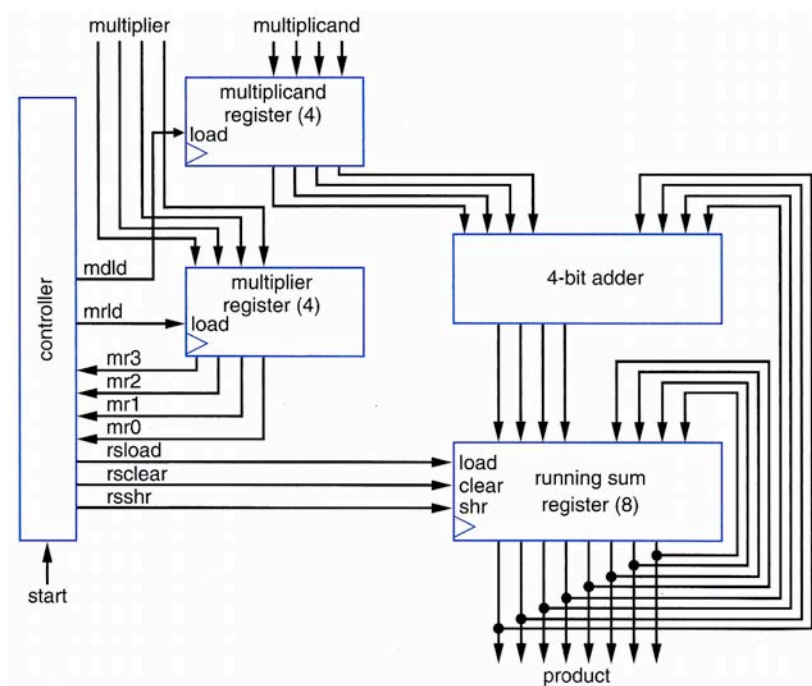

- Inputs: multiplicand ( $x$ ), multiplier ( $y$ )
- Outputs: product ( $z$ )

## FSM Diagram:

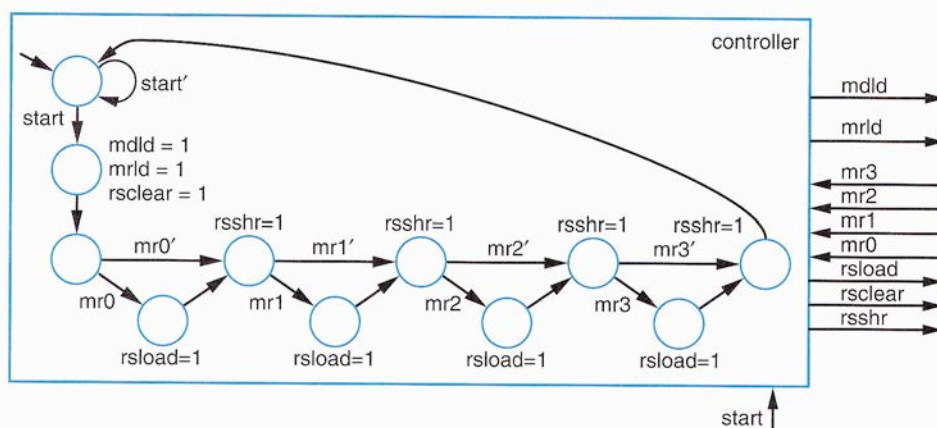

Note: FSM diagrams for the register and adder components not included to avoid redundancy. Only the FSM for the controller above is necessary for this project.

## FPGA Specifications:

- $SW[7:4]$  = Multiplicand, Binary (4-bit)
- $SW[3:0]$  = Multiplier, Binary (4-bit)
- $LD[7:0]$  = Product, Binary (8-bit)
- $AN[3:0]$  = Product, Decimal\*

\* = Denotes that implementing this function is optional.

## Schedule:

<u>Task</u>	<u>Deadline</u>
Adder / Registers / Controller	April 18
Structural & Implementation	April 25