

# ECE 2700 Lab 2

**Due the week of 01/28 at the beginning of your registered lab session (100 points)**

## Objectives

To learn how to build, simulate, and implement simple combinational circuits in Verilog/Xilinx.

## 1 Pre-Lab Preparation

1. Construct truth tables for the circuits in Problem 2.52 from the main textbook.
2. Write Boolean equations for the digital system described in Problem 2.21 from the main textbook. Draw the corresponding circuits.

**Recall that you will not get the pre-lab credit if the prep work is not finished prior to your assigned lab time.**

Note that it may be useful to bring Lab 1 instructions, Taylor's Verilog tutorial, and the secondary text to lab for reference. Pay close attention to Chapter 6, which is a Verilog mini-reference. Also, the example on page 34 shows how to use the **built-in** logic gates in Verilog.

## 2 Overview

In this lab, you will implement some simple combinational digital systems in Verilog, simulate your designs, and implement one of the systems on the Basys board.

## 3 Part I

You will use simulations to determine if the two circuits in Problem 2.52 are equivalent. Create a new directory called **Lab2** inside the **ECE2700** directory you created last week. Start Xilinx ISE and create a new project called **CircuitsComparison** with 3 new files: **circuit1.v**, **circuit2.v**, and **testbench.v**. Make sure that you specify the files as Verilog files.

Implement the circuit on the left-hand side in **circuit1.v** and the circuit on the right-hand side in **circuit2.v** using built-in gates. Inside **testbench.v**, put in all possible test cases. Hint: there are 16 possible combinations.

Check for syntax errors and simulate your circuits. Verify the outputs and show the results to your TA. Are the circuits equivalent?

## 4 Part II

In the second part of the lab, you will implement the digital system described in Problem 2.21 and load it on the Basys board.

Create a new project titled `disco_system`. You will want to create two new files to add to this project: `ds_system.v`, which will contain your Verilog code and `disco_test.v`, which will contain your test cases.

Inside the file `ds_system.v`, write out the Verilog code to implement the disco system described in Problem 2.21 using built-in logic gates. Once you are done, write out all the possible test cases to `disco_test.v`. Each test vector should be simulated for 10 ns.

Check for any syntax errors and simulate your system. Show your results to the TA.

Create a UCF file. Locate `SW0` and `SW1` on the Basys board. `SW0` and `SW1` will correspond to the inputs `S` (sound sensor) and `M` (motion sensor), respectively. `LD0` and `LD1` will correspond to the outputs `L` (light) and `B` (ball), respectively. Perform appropriate pin assignments in the UCF file and take the steps necessary to load your design on the Basys board. Show your working design to the TA.

## 5 TA Checkoff

- (10 points) Complete pre-lab work prior to start of the lab.
- (30 points) Correct implementation of the two circuits (including exhaustive test cases).
- (30 points) Correct implementation of the disco system (including exhaustive test cases).
- (30 points) Disco system correctly working on the Basys board.